
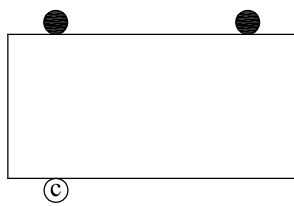


# Circuit Diagramming Exercises


## 7. 3-Way Circuit #2

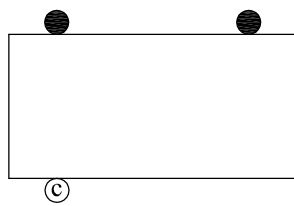

3-Way Switch




3-Way Switch

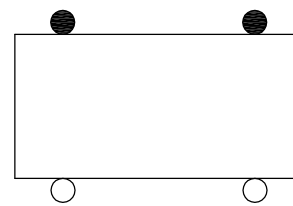


Switched Duplex

◀ Source


## 8. 3-Way Circuit #3

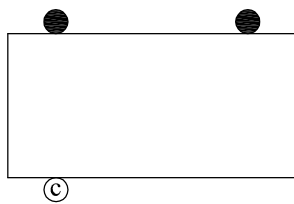

3-Way Switch

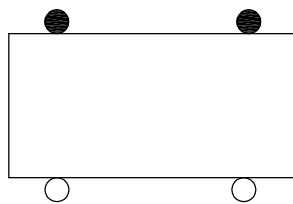


Switched Duplex

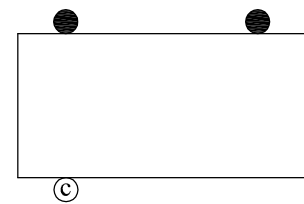


3-Way Switch

Source ▲

## 9. 1/2 HOT : 1/2 Switched Duplex

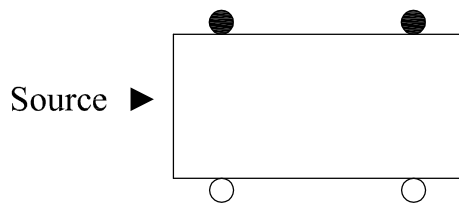


Top Switched  
Bottom Hot

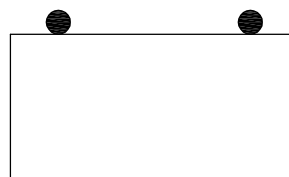


SPST Switch

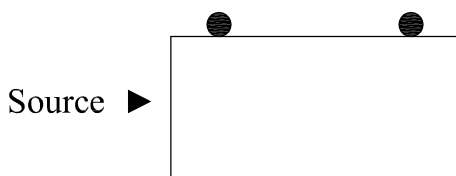
## 10. Switch to Control Two Duplex Receptacles



SPST Switch

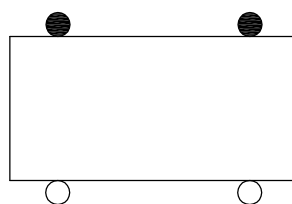

Switched Duplex

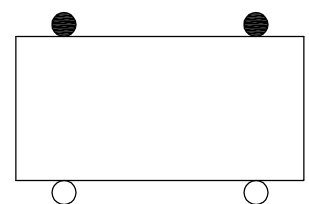

Switched Duplex